

[This question paper contains 4 printed pages.]

Your Roll No.....

Sr. No. of Question Paper : 1566

G

Unique Paper Code : 2512012302

Name of the Paper : Analog Electronics II

Name of the Course : **B.Sc. (H) Electronics**

Semester : III

Duration : 3 Hours

Maximum Marks : 90

Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. Question **1** is compulsory.
3. Attempt **Five** Questions in all.
4. Use of non-programmable scientific calculator is allowed.

1. (a) Explain why open loop configuration is unsuitable for linear applications. (3)

- (b) The output voltage of an op amp. changes by 10V in 2 μ s. Determine the slew rate. What is the ideal value for 741 op-amp? (3)

P.T.O.

- (c) Define CMRR. For a given op-amp, $\text{CMRR} = 200000$ and differential gain $A_d = 10^5$. Determine the common mode gain A_{cm} in dB. (3)
- (d) Discuss limitations of a basic differentiator and how it is removed. (3)
- (e) What are characteristics of comparators and its limitations? (3)
- (f) What are two basic modes in which the 555 Timer operates? Specify one application each for both the modes. (3)
2. (a) Derive expression for voltage gain (A_f), input resistance (R_{if}), output resistance (R_{of}) and bandwidth (f_p) of inverting amplifier using op-amp. (8)
- (b) How inverting amplifier is modified as current to voltage converter? Give its circuit. (4)
- (c) Explain and draw block diagram of an op-amp. Also draw the voltage transfer curve of an op-amp (Assume output offset voltage is zero). Compare any four characteristics of ideal op-amp with Op-amp 741. (6)
3. (a) Derive Total output offset voltage (V_{oot}) due to input offset voltage (V_{io}) and input bias current I_b for a closed loop inverting amplifier. (6)

- (b) Derive an expression for magnitude of gain and phase for open loop configuration of op amp using high frequency equivalent model. Also plot its frequency response. (6)
- (c) Design a subtractor using operational amplifier in difference amplifier mode. (6)
4. (a) Derive the expression for output voltage of basic integrator using op-amp. What are the limitations of a basic integrator circuit? Explain with the help of circuit how do we overcome these limitations in a practical integrator. (6)
- (b) Design an integrator circuit that can integrate a signal between frequency 1KHz to 10KHz. Also draw and explain its frequency response. (6)
- (c) Design a circuit using operational amplifier to implement
- $$V_o = - (V_a + V_b + V_c + V_d) / 4 \quad (6)$$
5. (a) Draw the schematic diagram of a square wave generator and explain its working with respect to its output response. (6)
- (b) Design a monostable multivibrator to be used as a divide by 2 frequency network. The frequency of the input trigger signal is 5kHz. Also draw its circuit. (6)

- (c) Design a Phase Shift Oscillator to generate a wave of frequency 500Hz. Also draw its circuit. (6)
6. (a) Explain working of 555 timer in astable multivibrator mode using circuit. (6)
- (b) Design a first-order high-pass filter having a cutoff frequency of 4 KHz and pass-band gain of 4. Draw its circuit and frequency response. (6)
- (c) What is an all-pass filter? Derive the expression for its voltage gain and phase difference. Give its one application. (6)
7. (a) How is Schmitt trigger different from comparators? Explain the functioning of a Schmitt trigger. Derive expression for its hysteresis voltage equation. (6)
- (b) Explain the functioning of non-inverting comparator? Draw necessary waveforms. Why limiter circuit is preferred over comparator? (6)
- (c) Explain working of voltage limiter circuit with a p-n junction diode in its feedback path (Assume forward bias voltage drop as 0.7V). Draw output waveform with respect to input. Now replace p-n junction diode with zener diode and again draw output waveform with respect to input. (6)